 


VLSI LAB Digital Assignment 4

Submitted by:

Swarup Tripathy — 19BEE0167



School of Electrical Engineering

Faculty: Professor Balamurugan S

Course: EEE-4028

Course Name: VLSI Lab

Lab Slot: L43 + L44

This work is submitted in partial fulfilment of the requirement of the award of the degree of Bachelor of Technology in EEE

March 2, 2022

4-BIT WALLACE TREE MULTIPLIER

Objectives

1. To provide students with the background needed to design, develop, and test digital arithmetic circuits using IEEE standard Verilog HDL.
2. To provide an understanding complex arithmetic circuit design principles and its architecture design.

Outcomes

1. After completion of this course the students will be familiar with design and implementation of Digital Arithmetic building blocks using Verilog HDL and Modelsim Software.

AIM

1. Design a 4 bit wallace tree multiplier using 7 full adders and 8 half adders.


REQUIRED SOFTWARE

1. Model sim software for simulation
2. Microsoft Visio for making flowchart
3. Documentation to be done using \LaTeX

CIRCUIT DIAGRAM

WALLACE TREE MULTIPLIER

19BEE0167 – Swarup Tripathy

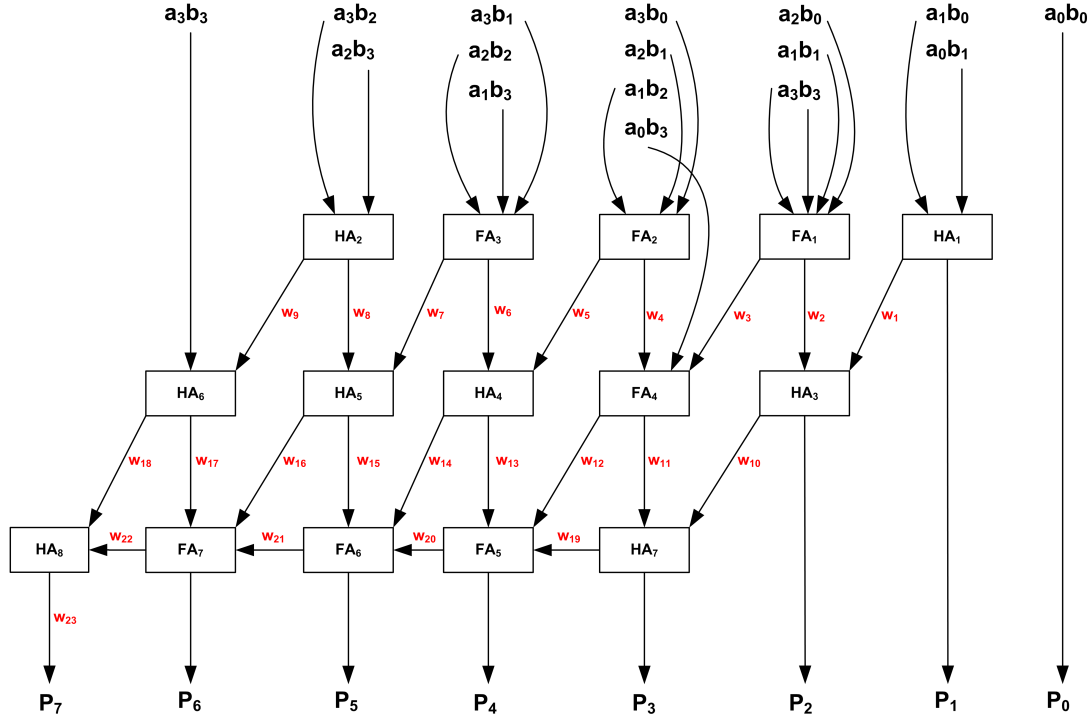

Design Code

1. Verilog Module — wallacedesigncode.v

```
module wallace_tree_19BEE0167(input [3:0]a,b,output [7:0]p);
wire [22:1]w;
assign p[0] = a[0]&b[0];
half_adder ha1((a[1]&b[0]),(a[0]&b[1]),p[1],w[1]);
full_adder fa1((a[1]&b[1]),(a[0]&b[2]),(a[2]&b[0]),w[2],w[3]);
full_adder fa2((a[2]&b[1]),(a[1]&b[2]),(a[3]&b[0]),w[4],w[5]);
full_adder fa3((a[3]&b[1]),(a[2]&b[2]),(a[1]&b[3]),w[6],w[7]);
half_adder ha2((a[3]&b[2]),(a[2]&b[3]),w[8],w[9]);

half_adder ha3(w[1],w[2],p[2],w[10]);
full_adder fa4((a[0]&b[3]),w[4],w[3],w[11],w[12]);
half_adder ha4(w[5],w[6],w[13],w[14]);
half_adder ha5(w[7],w[8],w[15],w[16]);
half_adder ha6((a[3]&b[3]),w[9],w[17],w[18]);

half_adder ha7(w[10],w[11],p[3],w[19]);
full_adder fa5(w[12],w[19],w[13],p[4],w[20]);
full_adder fa6(w[14],w[15],w[20],p[5],w[21]);
```

```

full_adder fa7(w[16],w[17],w[21],p[6],w[22]);
assign p[7]=w[18]^w[22];
endmodule

```

2. Fulladder.v

```

module fa_df_19BEE0167(input a,b,cin,output sum,cout);
assign sum=a^b^cin;
assign cout=(a^b)&cin|(a&b);
endmodule

```

3. Halfadder.v

```

module half_adder(input a,b, output sum,cout);
xor x1(sum,a,b);
and a1(cout,a,b);
endmodule

```


4. Test Fixture — wallaceTest.v

```

module test_wallace_tree();
reg [3:0]a;
reg [3:0]b;
wire [7:0]p;
reg [7:0]check;
wallace_tree_19BEE0167 uut(.a(a),.b(b),.p(p));
initial repeat(10) begin
a = $random;
b = $random;
check = a*b;
#10;
$display($time,"%d*%d=%d(%d)", a, b, p, check);
end
endmodule

```

5. Output

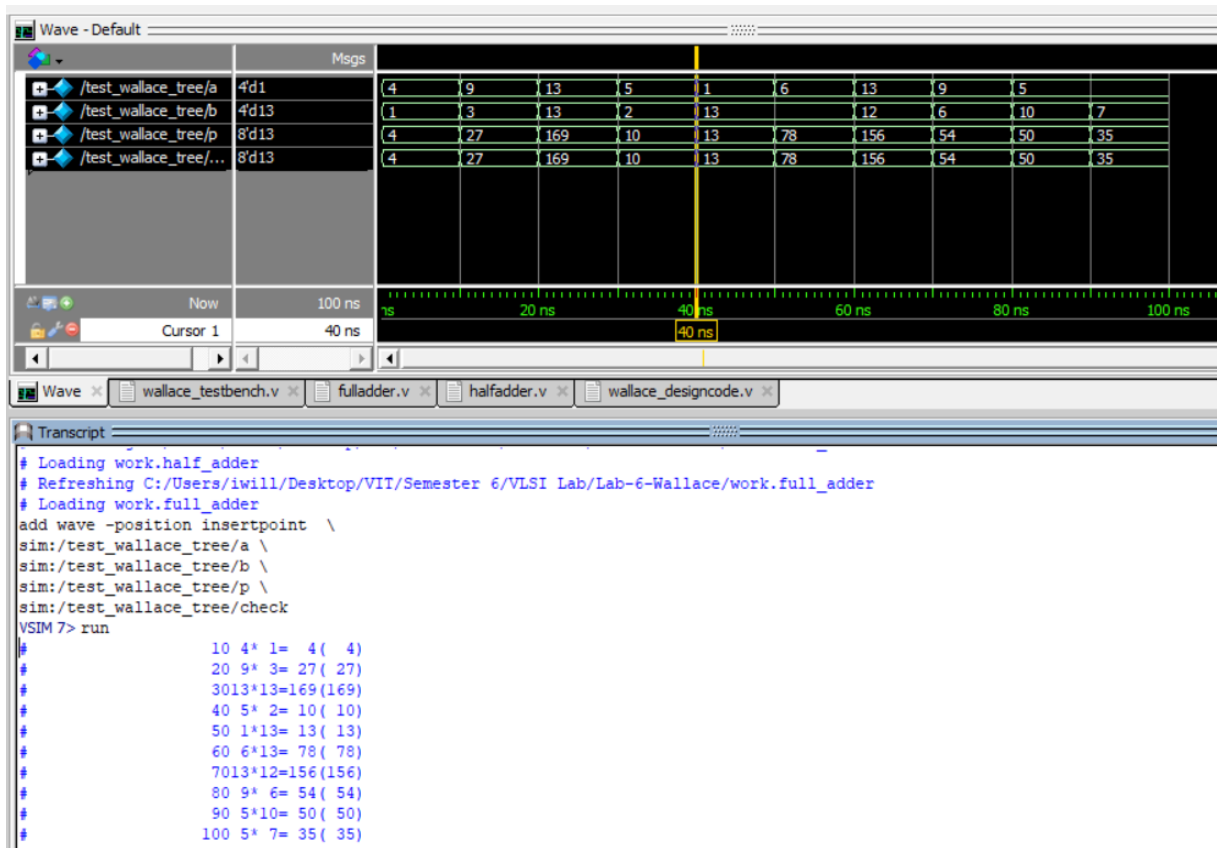

6. Console Output

```

# 10 4* 1= 4( 4)
# 20 9* 3= 27( 27)
# 30 13*13=169(169)
# 40 5* 2= 10( 10)
# 50 1*13= 13( 13)
# 60 6*13= 78( 78)
# 70 13*12=156(156)
# 80 9* 6= 54( 54)
# 90 5*10= 50( 50)
# 100 5* 7= 35( 35)

```

Result

1. Successfully the 4-bit wallace tree multiplier has been designed and the output was verified.

Inference

1. In this experiment learnt about how to construct multiple-bit adders.