 


# VLSI LAB Digital Assignment 2

Submitted by:

**Swarup Tripathy — 19BEE0167**



**School of Electrical Engineering**

**Faculty: Professor Balamurugan S**

**Course: EEE-4028**

**Course Name: VLSI Lab**

**Lab Slot: L43 + L44**

This work is submitted in partial fulfilment of the requirement of the award of the degree of Bachelor of Technology in EEE

February 27, 2022

# 4-BIT CARRY LOOK AHEAD ADDER

## Objectives

1. To provide students with the background needed to design, develop, and test digital arithmetic circuits using IEEE standard Verilog HDL.
2. To provide an understanding complex arithmetic circuit design principles and its architecture design.

## Outcomes

1. After completion of this course the students will be familiar with design and implementation of Digital Arithmetic building blocks using Verilog HDL and Modelsim Software.

## AIM

1. Design a 4 bit carry look ahead adder using four full adder circuit.


## REQUIRED SOFTWARE

1. Model sim software for simulation
2. Microsoft Visio for making flowchart
3. Documentation to be done using  $\text{\LaTeX}$

## CIRCUIT DIAGRAM

### CARRY GENERATION CIRCUIT

Swarup Tripathy - 19BEE0167

 

## Design Code

### 1. Verilog Module — cla.v

```
module cla_4bit_19bee0167(input[3:0]a,b,input cin,output[4:0]s);
    wire[3:0]p,g;
    wire[4:0]c;
    assign p=a^b;
    assign g=a&b;
    assign c[0] = cin;
```

```

assign c[1] = p[0]&c[0] | g[0];
assign c[2] = ((p[1]&p[0]&c[0]) | (p[1]&g[0]) | g[1]);
assign c[3] = ((p[2]&p[1]&p[0]&c[0]) | (p[2]&p[1]&g[0]) | (p[2]&g[1]) | g[2]);
assign c[4] = ((p[3]&p[2]&p[1]&p[0]&c[0]) | (p[3]&p[2]&p[1]&g[0]) |
(p[3]&p[2]&g[1]) | (p[3]&g[2]) | g[3]);
assign s[3:0] = p^c[3:0];
assign s[4] = c[4];
endmodule

```

## 2. Test Fixture — claTest.v


```

module cla_test_4bit_19bee0167;
reg [3:0] a,b;
reg cin;
reg [4:0] check;
wire [4:0] s;

cla_4bit_19bee0167 uut(a,b,cin,s);
initial repeat(10)
begin
a = $random;
b = $random;
cin = $random;
check = a+b+cin;
#10 $display($time,"%d +%d+%d=%d(%d)",a,b,cin,s,check);
end
endmodule

```

## 3. Output

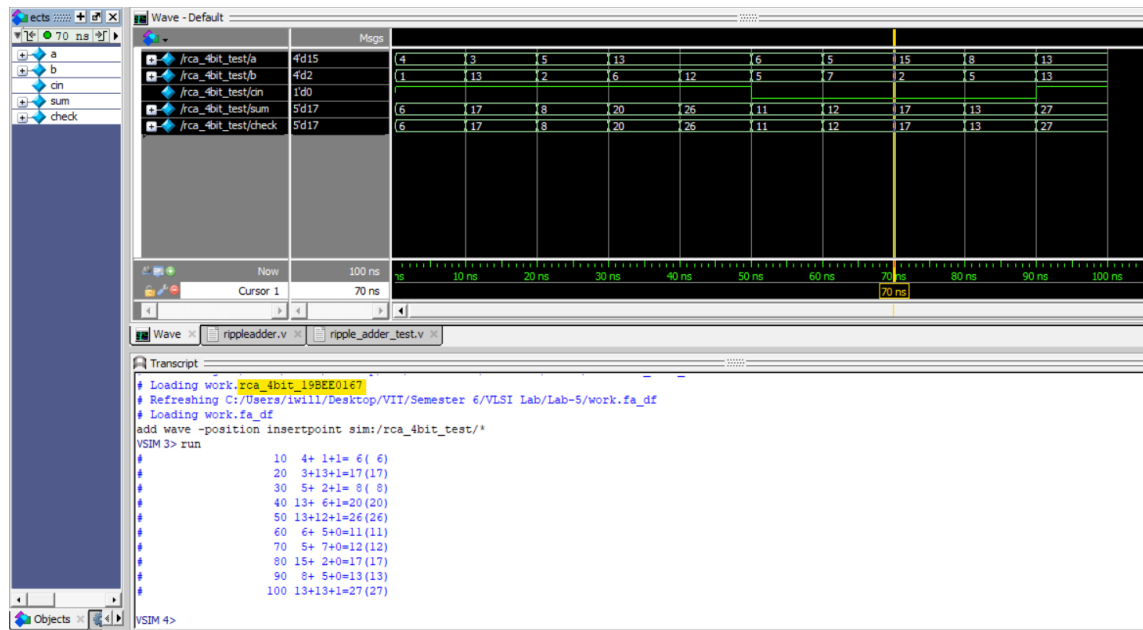

#### 4. Console Output

```

# 10 4 + 1+1= 6( 6)
# 20 3 +13+1=17(17)
# 30 5 + 2+1= 8( 8)
# 40 13 + 6+1=20(20)
# 50 13 +12+1=26(26)
# 60 6 + 5+0=11(11)
# 70 5 + 7+0=12(12)
# 80 15 + 2+0=17(17)
# 90 8 + 5+0=13(13)
# 100 13 +13+1=27(27)

```

## Result

1. Successfully the 4-bit carry look ahead adder has been designed and the output was verified.

## Inference

1. In this experiment learnt about how to construct multiple-bit adders.