 


VLSI LAB Digital Assignment 8

Submitted by:

Swarup Tripathy — 19BEE0167



School of Electrical Engineering

Faculty: Professor Balamurugan S

Course: EEE-4028

Course Name: VLSI Lab

Lab Slot: L43 + L44

This work is submitted in partial fulfilment of the requirement of the award of the degree of Bachelor of Technology in EEE

April 21, 2022

PIPELINED MAC DESIGN

Objectives

1. To provide students with the background needed to design, develop, and test digital arithmetic circuits using IEEE standard Verilog HDL.
2. To provide an understanding complex arithmetic circuit design principles and its architecture design.

Outcomes

1. After completion of this course the students will be familiar with design and implementation of Digital Arithmetic building blocks using Verilog HDL and Modelsim Software.

AIM

1. Design a pipelined mac design using 4bit, 8bit and 10 bit pipeline.


REQUIRED SOFTWARE

1. Model sim software for simulation
2. Microsoft Visio for making flowchart
3. Documentation to be done using \LaTeX

CIRCUIT DIAGRAM

MULTIPLIER AND ACCUMULATOR

Swarup Tripathy – 19BEE0167

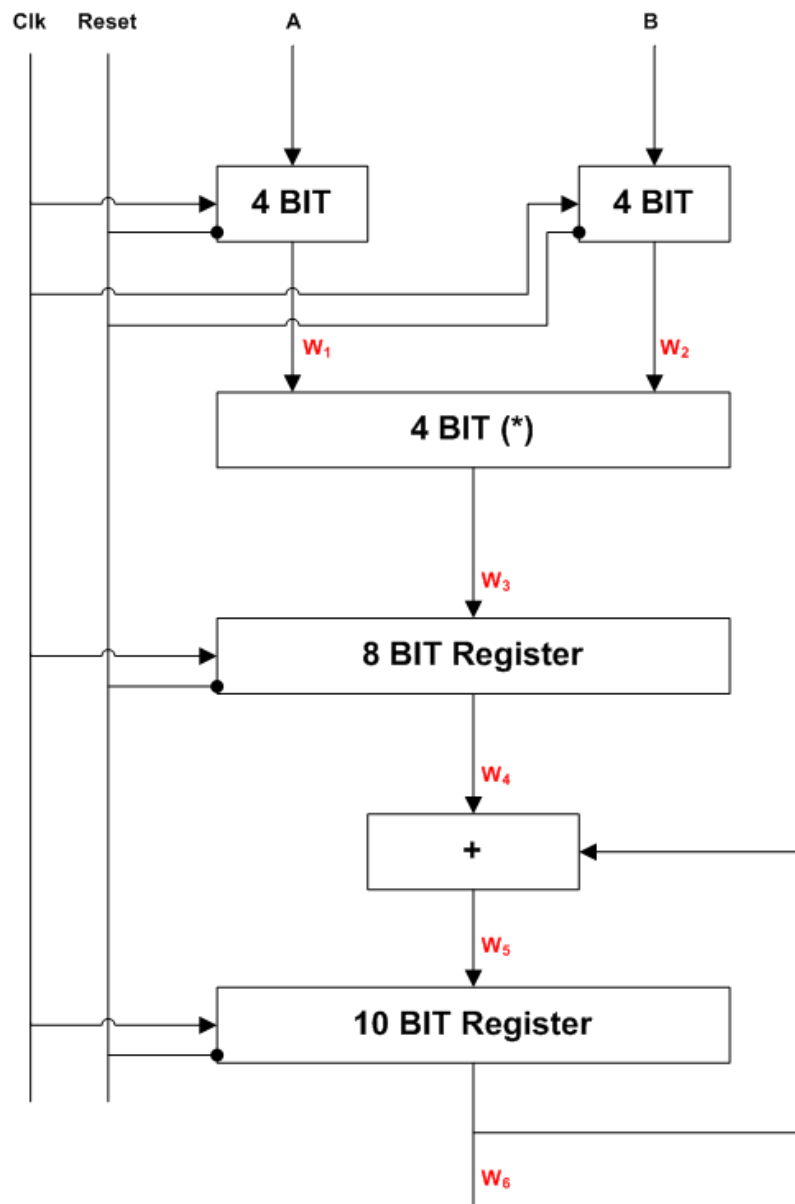

Design Code

1. Verilog Module — designcode.v

```

module pipeline_MAC(input clk, rst, input[3:0] a,b, output[9:0]y);
wire[3:0]w1,w2;
wire[7:0]w3,w4;
wire[9:0]w5,w6;
pipo_4b p1(clk, rst, a, w1);
pipo_4b p2(clk, rst, b, w2);
assign w3=w1*w2;
pipo_8b p3(clk, rst, w3, w4);
assign w5=w4+w6;
pipo_10b p4(clk, rst, w5, w6);
assign y=w6;
endmodule

```

2. pipo8bit.v

```

module pipo_8b(input clk, rst, input[7:0]d, output reg[7:0]q);
always@(posedge clk, negedge rst)
begin
if(!rst)
q<='b0;
else
q<=d;
end
endmodule

```

3. pipo10bit.v

```

module pipo_10b(input clk, rst, input[9:0]d, output reg[9:0]q);
always@(posedge clk, negedge rst)
begin
if(!rst)
q<='b0;
else
q<=d;
end
endmodule

```

4. pipo4bit.v

```

module pipo_4b(input clk, rst, input[3:0]d, output reg[3:0]q);
always@(posedge clk, negedge rst)

```

```

begin
  if(!rst)
    q<='b0;
  else
    q<=d;
  end
endmodule

```


5. Test Fixture — Test.v

```


module pipeline_MAC_test();
  reg clk,rst;
  reg[3:0]a,b;
  wire[9:0]y;
  pipeline_MAC UUT(clk, rst, a, b, y);
  initial begin
    rst=1'b0;
    clk=1'b0;
    #5;
    rst=1'b1;
    a=4'b0100;
    b=4'b1010;
    #10;
  end
  always #5 clk=~clk;

```

6. Output

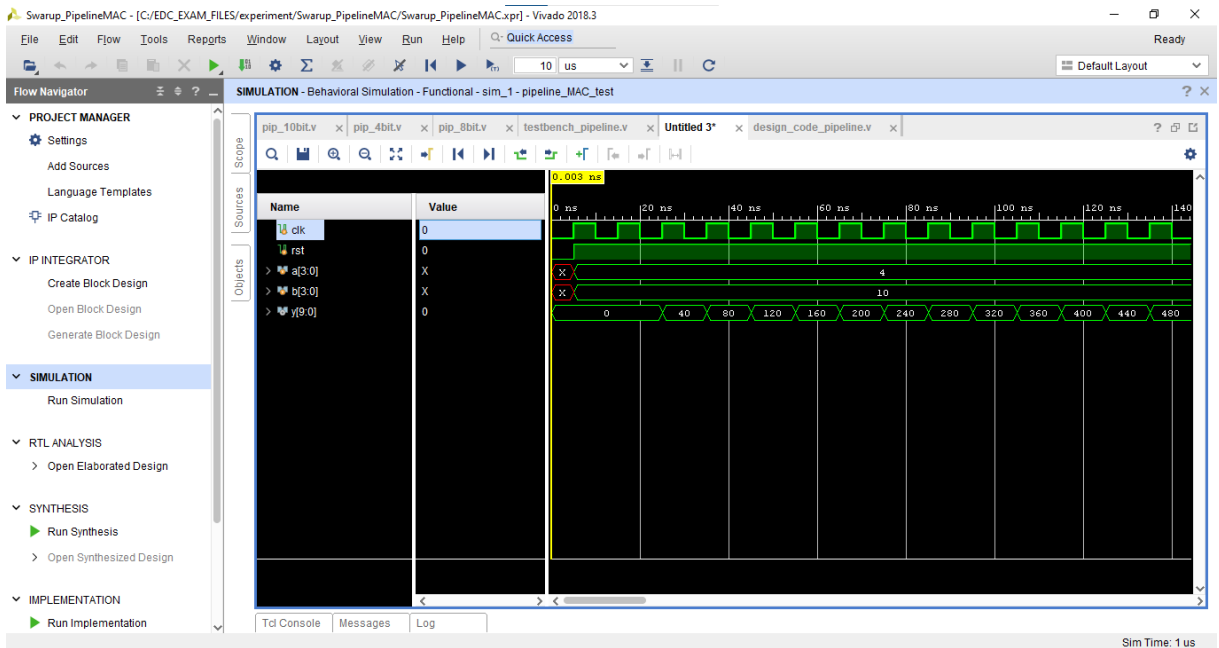

7. Console Output

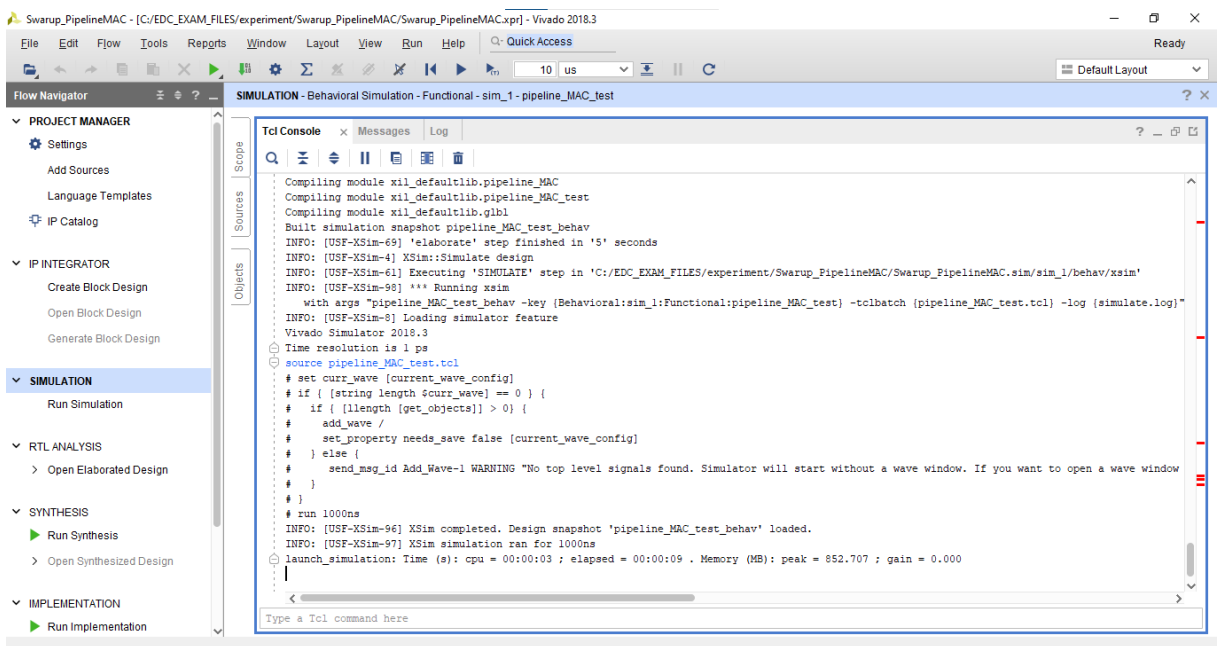


Result

1. Successfully the pipeline mac multiplier has been designed and the output was verified.

8

Multiplexer and Accumulator

$$y = ab + c$$

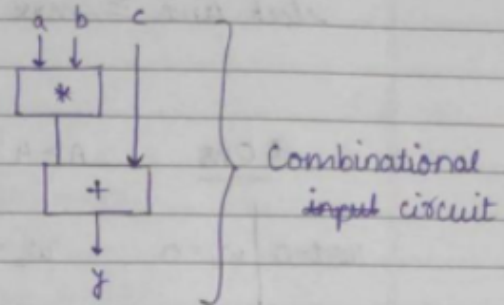


- To introduce a pipeline
- whenever performing addition we don't accept the input of a & b
- multiple execution are implemented in an overlapped manner

$$A = 4 \quad b = 5$$

$$@ 50 \text{ ns} \quad 4 \times 5 = 20$$

when pipelined

 - 3 bit register min required for i/p a and b



- growing size register depends on the resistor

- 4bit multiplier results in 8 bit.

- whenever using a resistor, we require a reset signal, for each resistor

clock → To trigger a signal

clock time \geq max of multiplication, Address

@ Ops $A=4$; $B=5$

reset=0 | $w_1=0$ $w_2=0$ $w_3=0$ $w_4=0$ $w_5=0$ $w_6=0$

• → represents a reset signal

needs to be 0

reset = 1, \uparrow | $w_1=4$ $w_2=5$ $w_3=20$ $w_4=0$
 $w_5=0$ $w_6=0$

↑ pulse | a_0 b_0
 $w_1=4$ $w_2=5$ $w_3=20$ $w_4=20$
 $w_5=20$ $w_6=0$
 $(a_0 \cdot b_0) \cdot 1$

we are keeping the reset @ 1, once becomes 0 will clear all the wires.

\uparrow | 4 5 20 20 20 20 $(a_1 b_1) \cdot 1$

\uparrow | 4 5 20 20 40 40 $(a_2 b_2) \cdot 1$

maximising the hardware efficiency

Parallel in
Parallel out

classmate

accumulation → previous value

CODE:

d is ip
q is o/p

```
module pp_4bit (input clk, reset,
                input [3:0] d,
                output reg [3:0] q)
```

```
always @ (posedge clk, negedge reset)
```

```
if (!reset) // reset = 1b'0
    q <= 4'b0000; q <= 4'b0000
```

```
else
```

```
q <= d;
```

```
end
```

```
endmodule
```

= Blocking
 <= non blocking

Transistor Sizing

- sizing of transistors to balance performance


```
module pipelined-MAC (input clk, reset, input [3:0] a, b,
                      output [9:0] y)
```

$(a + \bar{a}) * (b + \bar{b})$

```
  wire [3:0] w1, w2;
```

```
  wire [7:0] w3, w4;
```

$(a + \bar{a}) * (b + \bar{b})$

```
  wire [9:0] w5, w6;
```

```
  pip-4bit p1 (clk, reset, a, w1);
```

```
  pip-4bit p2 (clk, reset, b, w2);
```

```
  assign w3 = w1 * w2;
```

NOT AND OR plus

combinational logic implementation

```
  pip-8bit p3 (clk, reset, w3, w4);
```

```
  assign w5 = w4 + w6;
```

```
  pip-10bit (clk, reset, w5, w6);
```

```
  assign y = w[6];
```

```
endmodule
```

TESTBENCH

```
module pipelined-mac_test ();
```

```
  reg clk, reset;
```

```
  reg [3:0] a, b;
```

```
  wire [9:0] y;
```

```
  pipelined-MAC uut (
```

```
    * clk (clk),
```

```

        • reset (rst),
        • a(a),
        • b(b),
        • y(y))
    initial begin
        reset = 1'b0;
        clk = 1'b0;
        #5
        reset = 1'b1;
        a = 4'b0100;
        b = 4'b1010
        #10
    end
    always #5 clk = ~clk;
endmodule

```

PIP 4 BIT

```

module pip_4b(input clk, rst, input [3:0] d, output reg [3:0] q),
always @ (posedge clk, negedge rst)
begin
    if (!rst)
        q <= 'b0;
    else
        q <= d;
    end
endmodule

```

PIP 8 bit

```

module pip_8b(input clk, rst, input [7:0]d, output reg[7:0]q);
always@ (posedge clk, negedge rst)
begin
if (!rst)
q <= 'b0;
else
q <= d;
end
endmodule


```

PIP 10 BIT

```

module pip_10b(input clk, rst, input [9:0]d, output reg[9:0]q);
always@ (posedge clk, negedge rst)
begin
if (!rst)
q <= 'b0;
else
q <= d;
end
endmodule

```

 

Inference

1. In this experiment learnt about how to construct pipelined MAC design.